

# Computer Architecture and Organisation

## Lecture 1

Bert Molenkamp

### Learning objectives:

- You can design combinational logic
- You understand the principles of a synchronous sequential system

1

---

### IEEE (EE) / “pearls” (CSC):

- Logic gates
- Boolean algebra
- Truth table

### Today:

- Standard form (SOP form)
- Karnaugh-map
- Example combinational logic
  - Truth table, Karnaugh-map, minimal SOP-form
- Asynchronous, Synchronous sequential logic
- Memory elements

2

2

## Overview of binary functions of two variables

Name	Distinctive shape	Rectangular shape	Algebraic equation	Truth table															
AND			$F = X \cdot Y$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	X	Y	F	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR			$F = X + Y$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
NAND			$F = \overline{A \cdot B}$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOR			$F = \overline{X + Y}$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
Exclusive-OR (XOR)			$F = X \cdot \bar{Y} + \bar{X} \cdot Y$ $F = X \oplus Y$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
Exclusive-NOR (XNOR)			$F = X \cdot Y + \bar{X} \cdot \bar{Y}$ $F = \overline{X \oplus Y}$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	

3

3

## Basic properties of Boolean algebra (more on page 438)

$A \cdot B = B \cdot A$	$A + B = B + A$	Commutative
$A(B + C) = A \cdot B + A \cdot C$	$A + B \cdot C = (A + B) \cdot (A + C)$	Distributive
$1 \cdot A = A$	$0 + A = A$	
$A \cdot \bar{A} = 0$	$A + \bar{A} = 1$	
$0 \cdot A = 0$	$1 + A = 1$	
$A(B \cdot C) = (A \cdot B)C$	$A + (B + C) = (A + B) + C$	Associative
$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \cdot \bar{B}$	DeMorgan (often used)

DeMorgan theorem also for more than 2 variables, e.g.

$$\overline{A \cdot B \cdot C} = \bar{A} + \bar{B} + \bar{C} \quad \overline{A + B + C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$

In a design we use names, e.g. CLK. Therefore use explicitly the '·' symbol: A·B (not AB).

4

4

---

Logic symbols:

**not a** is also represented as  $\bar{a}$ ,  $a'$ ,  $!a$ ,  $\#a$ ,  $\neg a$   
**a and b** is also represented as  $a \cdot b$ ,  $a \& b$ ,  $a \wedge b$   
**a or b** is also represented as  $a + b$ ,  $a \vee b$   
**a xor b** is also represented as  $a \oplus b$ ,  $a \underline{\vee} b$

5

5

---



**NAND/NOR gate faster/less area than AND/OR gate**

---

$$F = a \cdot \bar{b} + c$$

Give a realization with only:

- NAND gates
- NOR gates

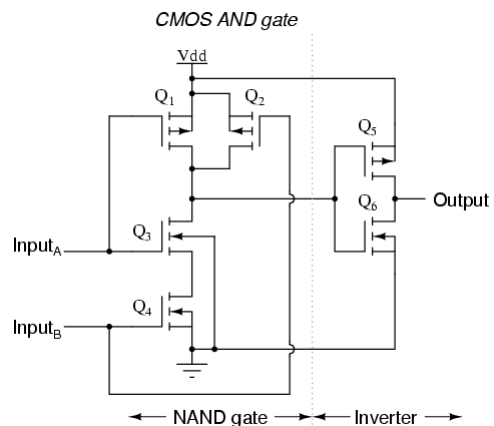 

[http://www.allaboutcircuits.com/vol\\_4/chpt\\_3/7.html](http://www.allaboutcircuits.com/vol_4/chpt_3/7.html)  
(not part of course)

6


6

## NAND (algebraic and schematic approach)

$$F = a.\bar{b} + c$$

$$F = \overline{\overline{a.\bar{b} + c}}$$

$$F = \overline{a.\bar{b}.\bar{c}}$$

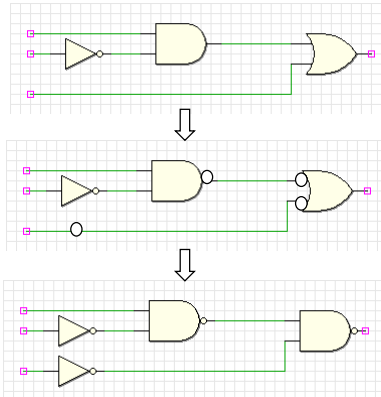

From output to input: replace with NAND gates using inverters.

An inverter is a NAND gate with input connected to each other

7

7

## Standard forms for combinational logic

### ◦ Two standard forms:

- SOP; Sum-of-Products
- POS; Product-of-Sums (part of Digital Hardware (EE))

### ◦ SOP

- A sum of product terms; OR of AND terms.
- A variable in the AND term is true or its complement (NOT) is true.
- A **minterm** is a product term with exactly one instance of every variable

$$F(A, B, C) = \bar{A} \cdot \bar{B} + \bar{B} \cdot C + \underbrace{A \cdot B \cdot \bar{C}}_{\text{minterm}}$$

$$F(A, B, C) = \overline{\bar{A} \cdot \bar{B}} + A \cdot B \cdot \bar{C}$$

Not product term → not SOP form

8

8

## More 'complex' components (Medium scale integration)



Often more complex components are used, e.g.:

- Multiplexer
- Demultiplexer
- Decoder
- Priority encoder
- Programmable logic (EE-students; "digital hardware")

9

9

## Multiplexer

 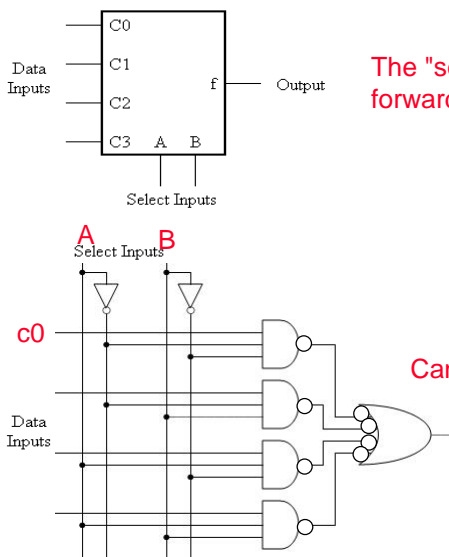


10

10

## Can you realize this function with a multiplexer?

$$F = a \bullet \bar{b} + c$$

 

Mux


A B Output

0 0 C0

0 1 C1

1 0 C2

1 1 C3

 


With  $a=1$ ,  $b=0$   $F=1 \rightarrow C2=1$ , other inputs  $c$

11

11
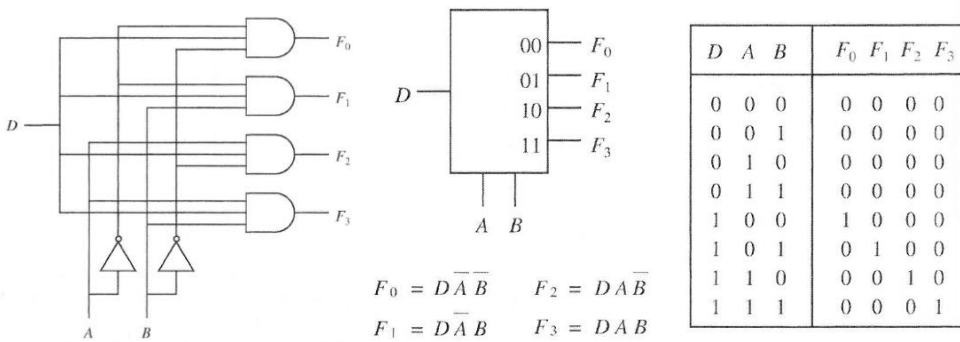
## Demultiplexer (inverse of multiplexer)




$$F_0 = D\bar{A}\bar{B} \quad F_2 = DA\bar{B}$$

$$F_1 = D\bar{A}B \quad F_3 = DAB$$

12

12

## Decoder

 


- The select inputs (S) determines which output is 1 (other outputs 0).
- $m\langle nr \rangle$  is a minterm.  
E.g. Output  $m_3$  is 1 when  $s_2=0, s_1=1$  and  $s_0=1$  ( $011_2=3_{10}$ )
- A decoder can also have an enable input (see book pag 451). When disabled all outputs are 0
- An application of a decoder: it can be used to extend the address range of a memory bank (CAO wk 3 & 4)

13

13

## Priority encoder

 

Inputs								Outputs		
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1

X = dont care



[http://www.electronics-tutorials.ws/combination/comb\\_4.html](http://www.electronics-tutorials.ws/combination/comb_4.html)

- The binary encoded output has the value of the first ( $D_7 \dots D_0$ ) input that is 1.
- A priority encoder can be used for arbitration between devices that compete for the same resource (CAO wk 3 & 4).

14

14

  **Give a simplified SOP-form for this circuit.**



a	b	c	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Find simplified SOP-form using:


- Algebraic reduction
- Karnaugh map reduction
- With truth table? Rarely!

$$\bar{F} = a.b.c$$

$$F = \overline{a.b.c}$$

$$F = \bar{a} + \bar{b} + \bar{c}$$

**Algebraic reduction.**

 

$$F = \overline{A.B} + \overline{B.C} + \overline{B.C}$$

$$F = \overline{A} + \overline{B} + \overline{B.C} + \overline{B.C} \quad \text{DeMorgan}$$

$$F = \overline{A} + \overline{B}.1 + \overline{B.C} + \overline{B.C}$$

$$F = \overline{A} + \overline{B}.(C + \overline{C}) + \overline{B.C} + \overline{B.C}$$

$$F = \overline{A} + \overline{B}.C + \overline{B.C} + \overline{B.C} + \overline{B.C}$$

$$F = \overline{A} + \overline{B}.C + \overline{B.C} + \overline{B.C}$$


$$F = \overline{A} + \overline{B}.C + \overline{B.C} + \overline{B.C} + \overline{B.C}$$

$$F = \overline{A} + \overline{B}(C + \overline{C}) + (\overline{B} + B)\overline{C}$$

$$F = \overline{A} + \overline{B} + \overline{C}$$



## Karnaugh.

 


Gray code

		bc			
		00	01	b	
a	0	0	1	3	2
	1	4	5	7	6
		1	1	0	1
		c			

17

17

## Karnaugh.

 

Group adjacent cells!  
 2 cells → 1 variable less  
 4 cells → 2 variables less  
 8 cells → 3 variables less

Adjacent cells may not include 0

Adjacent cells are horizontal/vertical,  
 not diagonal


Each group of adjacent cells should  
 be as large as possible

Groups may overlap

18

18

## Karnaugh.

 

$$F = \bar{a} + \bar{b} + \bar{c}$$

19

19

## Example

- °  $F = 1$  for the prime numbers in the range 1 to 9
- °  $F = 0$  for non-prime numbers in the range 1 to 9

WX \ YZ	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

WX \ YZ	00	01	11	10
00	d	0	1	1
01	0	1	1	0
11	d	d	d	d
10	0	0	d	d

$$F(W,X,Y,Z) = \sum m(2,3,5,7) \quad d = \sum m(0,10,11,12,13,14,15)$$

20

20


## What is the SOP-solution?

**F**

WX \ YZ		Y			
		00	01	11	10
W	X	-		1	1
			1	1	
		-	-	-	-
				-	-

Green bars highlight the groups for the SOP solution: a bar under the top row (YZ=00, 01) and a bar under the bottom row (YZ=11, 10).

$$F = \bar{X} \cdot Y + X \cdot Z$$

 

For fields that are don't care often 'd', 'x' or '-' is used

21

21

## Combinatorial <-> Sequential

### Combinational logic

- Has no memory
- The outputs are functions of the **current** inputs.


### Sequential logic

- Can store data; has **memory**
- The outputs are functions of the **current** inputs and the **past**.

22

22

## SR-latch with NORs

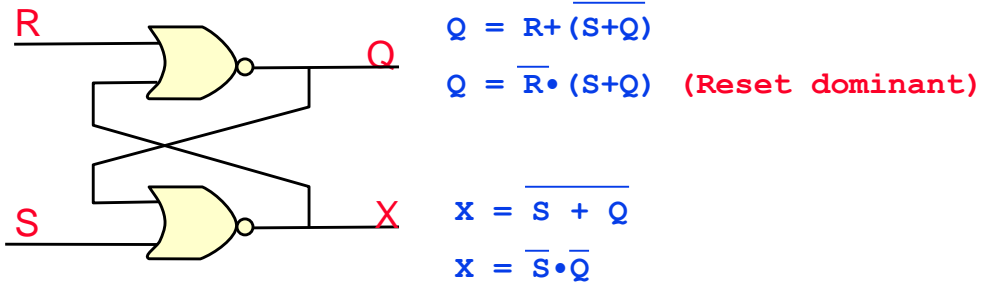

- Output  $Q$  is dominated by the Reset
- Output  $X$  is the inverse of  $Q$ , except when  $S=1, R=1$ , because the Set dominates  $X$ , hence  $X=0$  ( $S=1, R=1$  is often indicated as 'disallowed').
- $X$  is often indicated with  $\overline{Q}$ , although this is not correct
- An SR-latch with cross coupled NAND gates is also possible

23

23

## D-latch 1

- D-latch has two inputs,  $C$  (Control) and  $D$  (Data) and output  $Q$
- When  $C=0$  then  $Q=Q$  (remember)
- When  $C=1$  then  $Q=D$  (follow input D)

C	D	Q
0	0	Q
0	1	Q
1	0	0
1	1	1


Q	C	D	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Q:

	C			
Q	0	0	1	0
Q	1	1	1	0

D

$$Q = C \cdot D + \overline{C} \cdot Q$$

 


24

24
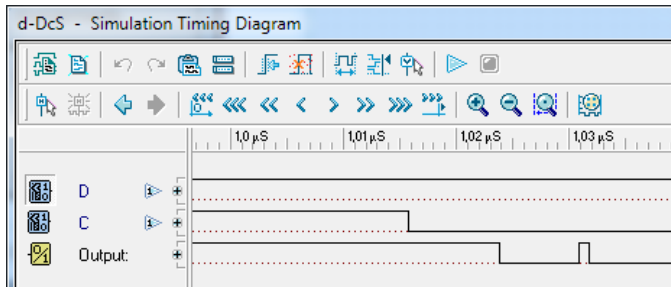
## D-latch 2

- The D-latch has a problem when  $D=1$  and there is a transition from  $C=1$  to  $C=0$
- The output  $Q$  should remain  $1$ , but due to the delays of the components the output is not what is expected.
- Beneath a simulation result with DEEDS (software on Canvas).
- Solution: add an extra, seemingly unnecessary, product term ( $Q \cdot D$ ) in the solution





25

25

## D-latch 3

	C			
Q:	0	0	1	0
Q	1	1	1	0
	D			
 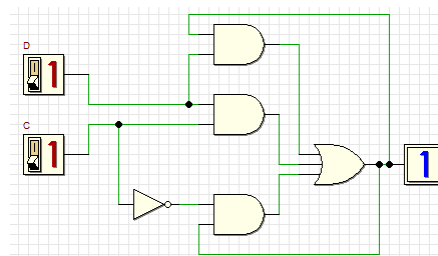
$$Q = C \cdot D + \overline{C} \cdot Q + D \cdot Q$$



26

26

## Asynchronous sequential circuits

- Memory is created with feedback
- This is called an **asynchronous sequential circuit**
- The signals fed back represent the **state** of the system.
- In principle any sequential circuit can be made this way.  
(No explicit memory elements)

27

27

## Problems of an asynchronous circuit

- It is **very difficult** to design reliable asynchronous circuits.
- Some causes are:
  - Differences in delay times. Not all bits of the state change at the same time. As a consequence arbitrary states can occur.
  - No synchronization: when is data "arrived"?
- Solution
  - Use explicit memory elements with a clock input
  - The memory devices are synchronized: they are all connected to a common clock, and the outputs can only change after a rising edge or falling edge of the clock (not on both edges of the clock)
  - The clock frequency is chosen sufficient low, such that all signals in the combinational logic are stable
- These circuits are called **synchronous sequential circuits** (abbreviated as **synchronous circuits**)

28

28

## Synchronous sequential circuits


- Almost all the larger digital circuits are **synchronous sequential circuits**; asynchronous techniques are rarely used.
- Synchronously sequentially actually means that the operation of parts of the circuit is **delayed** in such a way that even the slowest path into the circuit under the most unfavorable conditions of time, has sufficient time to stabilize before the next active edge of the clock.
  - This path is called “Critical path”
- All synchronous sequential circuits can be described using the following model.

29

29
 
## Model of a synchronous sequential system

- The current **Outputs (o)** are a function of the current **Inputs (I)** and the **Present State (s)**:  $I \times S \rightarrow O$
- The **Next State** is a function of the current **Inputs** and the **Present State**:  $I \times S \rightarrow S$
- This model is called: **Mealy** machine (output also depends on current inputs).



30

30

## Latches? flip-flops!

---


- Are D-latches suitable as memory element in this model?
- No!
  - As long as  $C=1$  the latches behave as “wires”.
  - Only if  $C$  is  $1$  for a short moment it could work; this is too critical
- Solution:
  - Do not use **latches**, use **flip-flops**. Flip-flops only change on an edge of the clock.

31

31

## Problem of D-latches


---

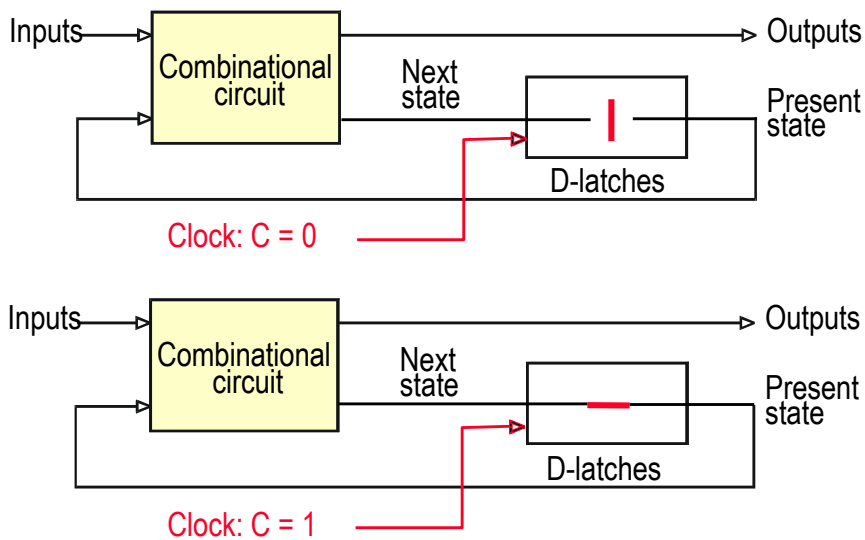

32

32

## Use flip-flops

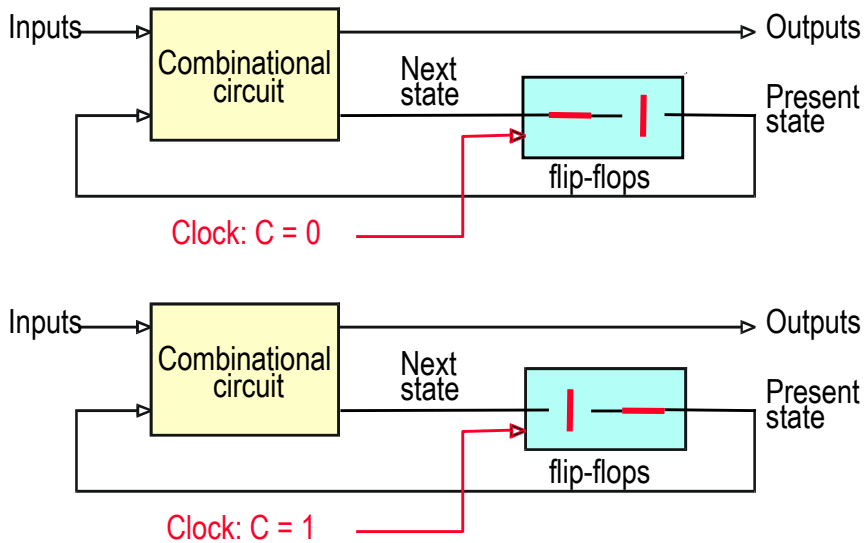

33

33

## flip-flops

- Edge sensitive clock input  $c$ , has a small triangle
- Active edge is rising edge of clock, unless the input has a circle (then the active edge is the falling edge)
- Clock input does not appear in descriptions and tables
- Current state is in tables denoted by  $Q(t)$  or  $Q$ ; next state with  $Q(t+1)$  or  $Q+$
- By far most commonly used is the D flip-flop; in addition also DE flip-flop, SR flip-flop, JK flip-flop and T flip-flop
- Output  $Q$  changes only on the active edge of the clock


34

34

## D flip-flop

D	Q+	
0	0	Reset
1	1	Set

 Next state is independent of current state




35

35
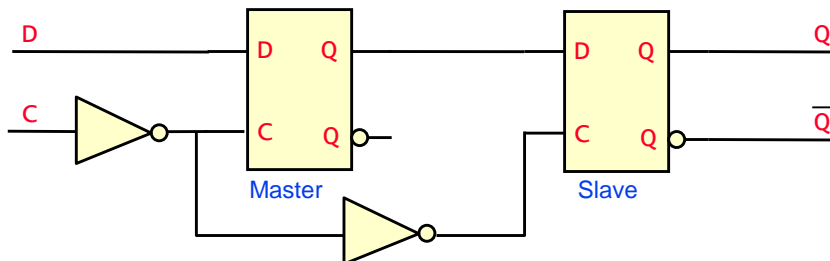
## D flip-flop realized with two latches

° Master-Slave principle

° In practice another implementation is used with the same behaviour but faster and smaller (not part of this course).



36


36

## DE flip-flop

- DE flip-flop is D flip-flop with enable **E**; when **E=0** flip-flop output is unchanged. When **E=1** flip-flop behaves as D flip-flop

E	D	Q+	
0	0	Q	Unchanged
0	1	Q	Unchanged
1	0	0	Reset
1	1	1	Set

Q	E	D	Q+	
0	0	0	0	Unchanged
0	0	1	0	Unchanged
0	1	0	0	Reset
0	1	1	1	Set
1	0	0	1	Unchanged
1	0	1	1	Unchanged
1	1	0	0	Reset
1	1	1	1	Set

 


37

37
 
## Asynchronous reset (R) and set (S)

- Flip-flops often have asynchronous clear (**R** or **CLR $\bar{N}$** ) and preset (**S** or **PR $\bar{N}$** ) inputs.
- These inputs are typically active low (indicated with a bubble at the input) and independent of the clock.
- These inputs can set or reset the flip-flop regardless of the status of the clock.
- These inputs are rarely used during normal operation, they are used to initialize the flip-flop.



38

38


## Timing

- A D flip-flop itself is an asynchronous sequential circuit.
- Hence the behaviour can also be unpredictable if timing constraints are not met (for EE students more detail in “Digital hardware”).
- Important timing constraints are:
  - **Tsu**: Setup time is the minimum amount of time the data signal should be held steady before the active edge of clock.
  - **Th**: Hold time is the minimum amount of time the data signal should be held steady after the active edge of clock
- **Tco**: The *clock to output delay* is the time required to obtain a valid output after the active edge of the clock.

39

39

## Example

 


- A more realistic waveform of the transition of the clock edge.
- In this example the hold time is **negative**.

40

40

## Example: shift register

 

- What is active edge of the clock?
- $T_{su} = 2\text{ns}$ ,  $T_h = 1\text{ns}$ ,  $T_{\text{propagation delay wires}} = 0\text{ns}$ 
  - When must the input *bit\_in* be stable?
  - What is the minimum  $T_{co}$  for a correct operation?
  - What is the maximum clock frequency (with minimum  $T_{co}$ )?

a) *bit\_in* stable: 2ns before falling edge of clock until 1 ns after falling edge of clock  
b) Input D of flipflop should be stable at least 1 ns after active edge  $\rightarrow T_{co} \geq 1\text{ns}$   
c) Max clock freq =  $1 / (T_{su} + T_{co}) = 1 / (3\text{ ns}) \sim 333\text{ MHz}$

41

41

- **What did you learn:**
  - You can design combinational logic
  - You understand the principles of a synchronous sequential system
- **Next lecture**
  - Finite state machines

42

42