

## Homework Lecture 2

### 1. Exercise A.28

“changes from 0 to 1” should be interpreted as the “in previous clock cycle the input was 0 (at active edge of clock) and the current input value is 1”. (Mealy FSM)

### 2. Exercise A.29

“last three bits” where the last bit is the current input value (Mealy FSM).


### 3. Exercise A.36

### 4. Exercise A37

(only SOP-form)

### 5. Exercise A.38


### 6. Exercise: 2 FF's in series

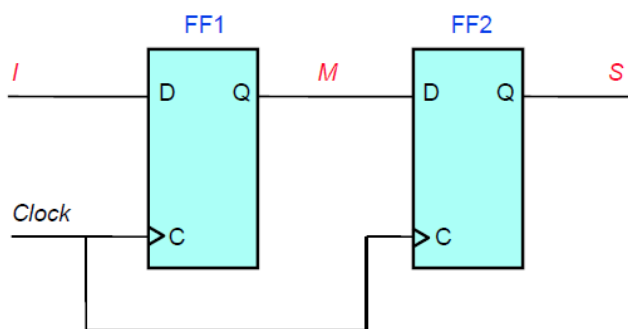

The timing properties of both flip-flops are:  $T_{su} = 6$  ns,  $T_h = -2$  ns,  $T_{co} = 3$  ns;

The wires have a delay of 0 ns.

 Draw the waveform for M and S (we assume ideal edges; instantaneously from  $0 \rightarrow 1$  and  $1 \rightarrow 0$ ). At 0 ns M and S are both 0.




## 7. Exercise: realize a DE flipflop

### DE flip-flop

° DE flip-flop is D flip-flop with enable **E**; when **E=0** flip-flop output is unchanged. When **E=1** flip-flop behaves as D flip-flop

E	D	Q+	
0	0	Q	Unchanged
0	1	Q	Unchanged
1	0	0	Reset
1	1	1	Set

 

Realize the DE flip-flop with a D flip-flop and combinational logic.

