
Computer Architecture and Organization

Arithmetic Datapath & Control

Lecture 4

1

1

Where are we?


- ▶ **What did you learn last week?**
 - ▶ You can design combinational logic (including Karnaugh map)
 - ▶ You can design synchronous sequential logic (including FSM)
 - ▶ You understand the different number representations
- ▶ **This week:**
 - ▶ **Today:**
 - You can perform simple arithmetic operations on unsigned and signed numbers and how it can be realized
 - You understand the components of a processor
 - ▶ **Tuesday:**
 - You can write programs in assembly for the ARC processor
 - ▶ **Wednesday:**
 - You understand the details of the data path and controller of the ARC processor

2

2

Multiple choice question

 - ▶ Try it yourself (do not discuss it with your neighbor)
- ▶ You have 10 seconds!
- ▶ What is the decimal value of pattern 1101
 - ▶ A: 13
 - ▶ B: -2
 - ▶ C: -3
 - ▶ D: -5
 - ▶ E: I don't know



3

3



Topics of this lecture

- ▶ **Unsigned/Signed addition** ↔
 - ▶ Ripple carry adder
 - ▶ Status signals
- ▶ **Unsigned Multiplication**
- ▶ **Components of a processor**
 - ▶ Datapath & Control
 - ▶ Register file
 - ▶ Shifter

4

4

Ripple-carry adder

  

- ▶ A full adder (FA) has 3 inputs (a, b, cin) and 2 outputs (s, cout)
- ▶ You can design the logic of a full-adder! How?
 - ▶ Truth-table → Karnaugh-map for the 2 outputs
→ 2 level logic (delay $\sim 2\Delta$)
- ▶ A chain of FA's is a ripple-carry adder.
 - ▶ What is the propagation delay of an N-bit ripple-carry adder?
 $\sim N \times 2\Delta$
(EE-students will reduce the delay by adding extra logic; week 5)

7


7

Addition of N-bit signed numbers

- ▶ Add two N-bit numbers and the result is N-bits.
- ▶ If the red line in the number circle is crossed the number can not be represented (overflow).

Bit position 1 →
 
$$\begin{array}{r}
 0\ 1\ 1\ (3) \\
 1\ 1\ 0\ (-2) \\
 \hline
 \text{x}\ 0\ 1
 \end{array}$$




- ▶ Bit position 1 generates a cout, therefore in bit position 2: 2^2 (=cout) + -2^2 (=sign bit) = 0 → X is 0
- ▶ Also a FA can be used for MSB position?
 - $s_2=0$ and $cout_2=1$ and ignore this $cout_2$
 - result is correct
- ▶ Again a ripple-carry adder! Same hardware as for **unsigned** numbers.
- ▶ How detect overflow?

8

8

Addition of N-bit signed numbers; cont'd
 
$$\begin{array}{r}
 0\ 1\ 1\ \quad (3) \\
 0\ 1\ 0\ \quad (2) \\
 \text{-----} + \\
 (0)\ 1\ 0\ 1\ \quad (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 1\ 1\ 1\ \quad (-1) \\
 1\ 0\ 0\ \quad (-4) \\
 \text{-----} + \\
 (1)\ 0\ 1\ 1\ \quad (3)
 \end{array}$$



- ▶ Carry-ripple adder is used. Cout is ignored.
- ▶ Addition of a positive number and a negative number cannot result in an overflow.
- ▶ Overflow when (see both examples):
 - ▶ Two positive numbers are added and the result is negative, or
 - ▶ Two negative numbers are added and the result is positive
- ▶ You can derive logic for the overflow detection
 - ▶ Truth-table → Karnaugh-map

9

9

Addition of 3-bit signed numbers: overflow

- ▶ Alternative detection of overflow using the carry bits
- ▶ Example: 3 bits numbers are sign extended (decimal value is not changed)

$$\begin{array}{r}
 1\ 1\ 1\ 1\ 1\ \quad \text{carry} \\
 ..\ 1\ 1\ 1\ 1\ 1\ 1\ 0\ \quad (-2) \\
 ..\ 1\ 1\ 1\ 1\ 1\ 1\ 1\ \quad (-1) \\
 \text{-----} + \\
 ..\ 1\ 1\ 1\ 1\ 1\ 0\ 1\ \quad (-3) \\
 \text{No overflow (N=3)}
 \end{array}$$

$$\begin{array}{r}
 0\ 0\ 0\ 0\ 0\ \quad \text{carry} \\
 ..\ 0\ 0\ 0\ 0\ 0\ 0\ 1\ \quad (1) \\
 ..\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ \quad (2) \\
 \text{-----} + \\
 ..\ 0\ 0\ 0\ 0\ 0\ 1\ 1\ \quad (3) \\
 \text{No overflow (N=3)}
 \end{array}$$

$$\begin{array}{r}
 0\ 0\ 0\ 0\ 1\ \quad \text{carry} \\
 ..\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ \quad (2) \\
 ..\ 0\ 0\ 0\ 0\ 0\ 1\ 1\ \quad (3) \\
 \text{-----} + \\
 ..\ 0\ 0\ 0\ 0\ 1\ 0\ 1 \\
 \text{Overflow (N=3)}
 \end{array}$$

$$\begin{array}{r}
 1\ 1\ 1\ 1\ 0\ \quad \text{carry} \\
 ..\ 1\ 1\ 1\ 1\ 1\ 1\ 0\ \quad (-2) \\
 ..\ 1\ 1\ 1\ 1\ 1\ 0\ 1\ \quad (-3) \\
 \text{-----} + \\
 ..\ 1\ 1\ 1\ 1\ 0\ 1\ 1 \\
 \text{Overflow (N=3)}
 \end{array}$$

- ▶ Overflow: Bit 2 of sum is not equal to bit 3 of sum (red)
 - ▶ Note: right most bit is Bit 0
- ▶ Overflow detection that is often used: cout1 ≠ cout2 (blue) (cout=carry out)
 - ▶ What is the logic for overflow detection?


10

10

Addition of numbers with different length

- ▶ Add these two signed numbers (20 sec)
 
$$\begin{array}{r} 1 0 1 \\ 0 1 0 1 0 \\ \hline + \end{array}$$



- ▶ Sign extend the shortest operand

$$\begin{array}{r} 1 1 1 0 1 \quad (-3) \\ 0 1 0 1 0 \quad (10) \\ \hline + \\ 0 0 1 1 1 \quad (7) \end{array}$$

11

11

Subtraction of signed numbers


- ▶ $A - B$ is equal to $A + (-B)$
- ▶ How can you determine $(-B)$?
 - ▶ Invert all bits of B (=1-complement) and add 1 (2-complement of B)

12

12

How does logic supports a program?
 
```
while (op1 < op2)
{ do something }
```




- ▶ **A program usually contains branches**
 - ▶ How can a processor check the condition: $op1 < op2$?
 - ▶ $op1 < op2 \equiv op1 - op2 < 0$
Perform the subtraction and check if the result is negative (status)! Based on the status the controller will instruct the data path.
- ▶ **The status bits (sufficient for this course)**
 - ▶ N (negative)
 - ▶ Z (zero)
 - ▶ V (oVerflow)
 - ▶ C (carry)

15

15


Ripple carry add/subtract with status

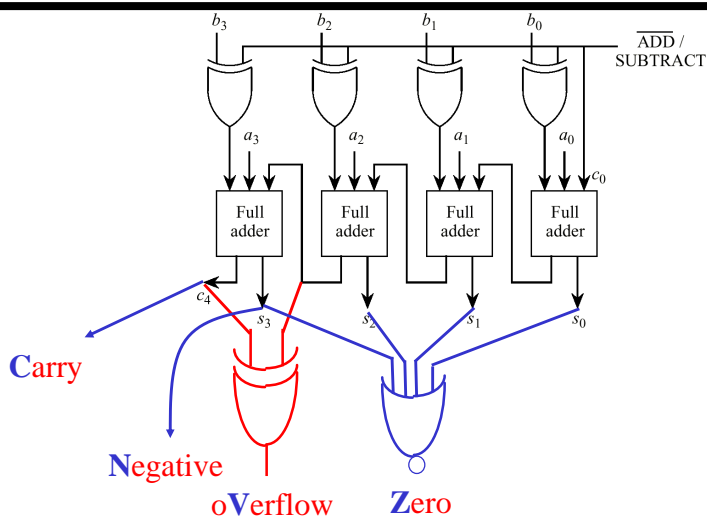

16

16

Incomplete simple processor

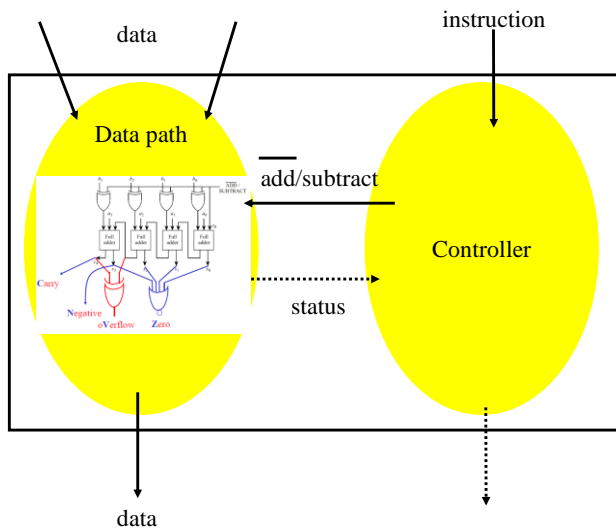

- ▶ **Data path**
 - ▶ Transport of data
 - ▶ Operation on data (add, and, shift,..)
 - ▶ Local storage of data (register file)
- ▶ **Controller**
 - ▶ Instructs the data path
 - ▶ Which operation?
 - ▶ and on which data?

17

17

Topics of this lecture

- ▶ Unsigned/Signed addition
- ▶ **Unsigned Multiplication** ⇄
- ▶ **Components processor**
 - ▶ Datapath & Control
 - ▶ Register file
 - ▶ Shifter

18

18

MULTIPLY (unsigned)

- ▶ Paper and pencil example (primary school ☺):

```
Multiplicand  1101
Multiplier   1011
-----
              1101
             1101
            0000
           1101
          -----
Product      10001111
```


- ▶ m bits \times n bits = $m+n$ bit product (no overflow)
- ▶ Binary makes it easy:
 - 0 \Rightarrow place 0000..0 (0 \times multiplicand)
 - 1 \Rightarrow place a copy multiplicand (1 \times multiplicand)
- ▶ 2 versions of multiply hardware & algorithm:
 - ▶ combinational / sequential (shift-add algorithm)

19

19

Unsigned **Combinational** Multiplier

Generate partial products

 

(c) 2005 - 2012 W. J. Dally

20

Unsigned **Combinational** Multiplier, cont'd

Sum up partial products

What is the max. propagation delay?


$$\sim \Delta + 6 \times 2\Delta \quad (t_{FA} \sim 2\Delta)$$

$$\sim \Delta + 2(N-1) \times 2\Delta$$

What is the area?

$N(N-1)$ FA's +


N^2 and-gates

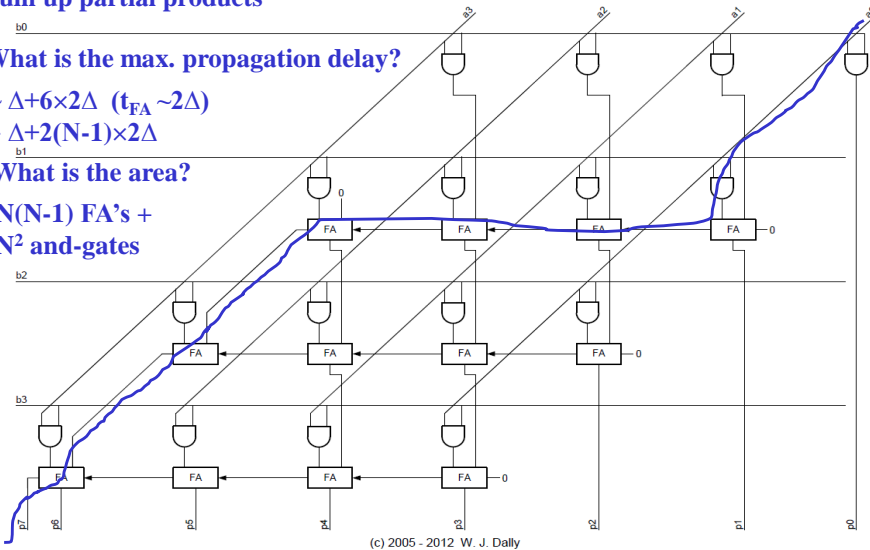

21

Sequential multiplier (shift-add method)

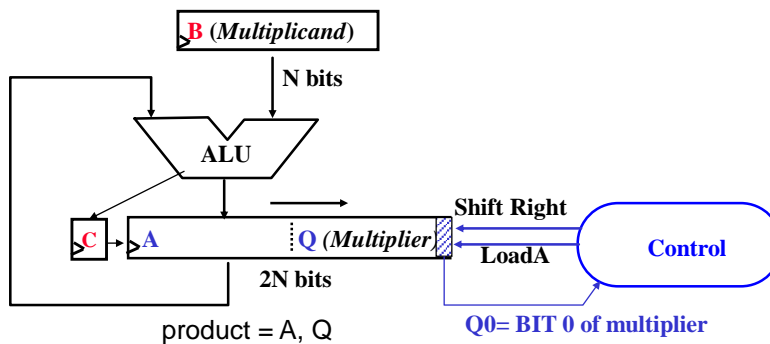- ▶ Multiplicand N-bits, lower N bits of product register (2N bits) is initially filled with the multiplier.
- ▶ If $Q_0=1$ (LSB) perform addition of multiplicand and higher N bits of product. Shift "C,A,Q" register one position to the right




22

22

Sequential multiplier (shift-add method)

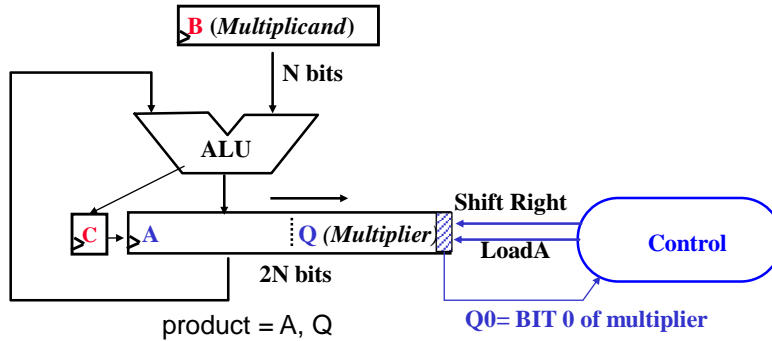- ▶ How many clock cycles?
 - ▶ 1 for initialization and $2N$ for the algorithm (assuming add and shift are not in the same clock cycle)
- ▶ Area?
 - ▶ 1 N-bit Adder (in ALU), registers and control logic



23

23

How multiply signed numbers?

- ▶ Size operands: m bits and n bits; result: m+n bit product (no overflow)
- ▶ For addition we can use the same hardware unsigned and signed numbers
- ▶ Can we use the same hardware for unsigned and signed multiplication?
- ▶ Why is this not correct?

$$\begin{array}{r}
 110 \\
 101 \\
 \hline
 110 \\
 000 \\
 110 \\
 \hline
 ?11110
 \end{array}$$

24

24

How multiply signed numbers? Cont'd

- ▶ Remember addition:
signed numbers with different length?
→ extend with sign bits
- ▶ MSB of multiplier has weight -2^2 .
You have to add:
→ $-2^2 \times$ multiplicand
→ $2^2 \times (-$ multiplicand)
→ $2^2 \times$ (two's complement of multiplicand)

$$\begin{array}{r}
 1\ 1\ 0 \\
 1\ 0\ 1 \\
 \hline
 \times \\
 1\ 1\ 1\ 1\ 1\ 0 \\
 0\ 0\ 0\ 0\ 0\ 0 \\
 0\ 0\ 1\ 0\ 0\ 0 \\
 \hline
 0\ 0\ 0\ 1\ 1\ 0 +
 \end{array}$$

- ▶ Easy isn't it?



Signed multiplication is not part of CAO.
Only remember that it is different from unsigned multiplication
EE students will use an alternative method in DH

25

25


Topics of this lecture

- ▶ **Unsigned/Signed addition**
 - ▶ Ripple carry adder
 - ▶ Status signals
- ▶ **Multiplication**
 - ▶ Unsigned
- ▶ **Components of a processor**
 - ▶ **Datapath & Control** ⇐
 - ▶ Register file
 - ▶ Shifter

26


26

Shift-add algorithm

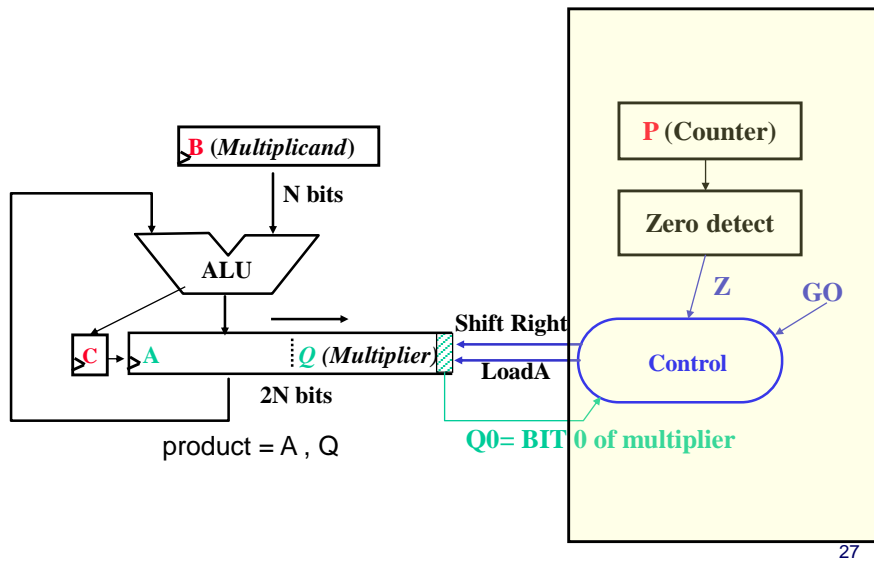

27


Datapath

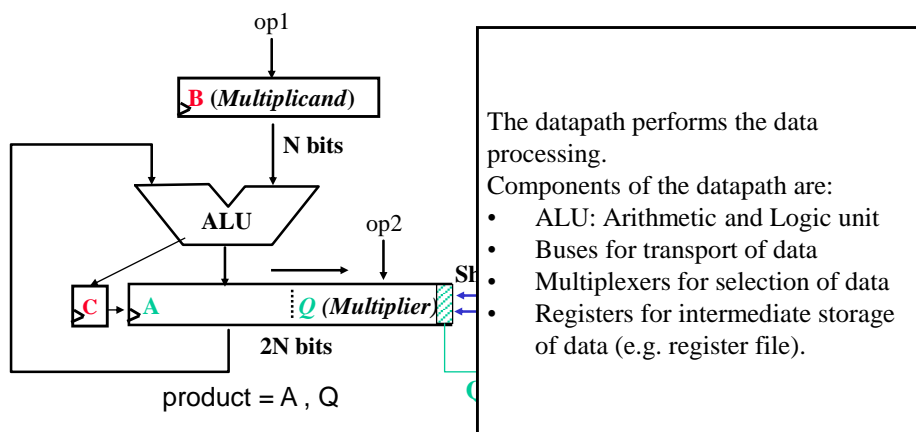

28

28

Controller

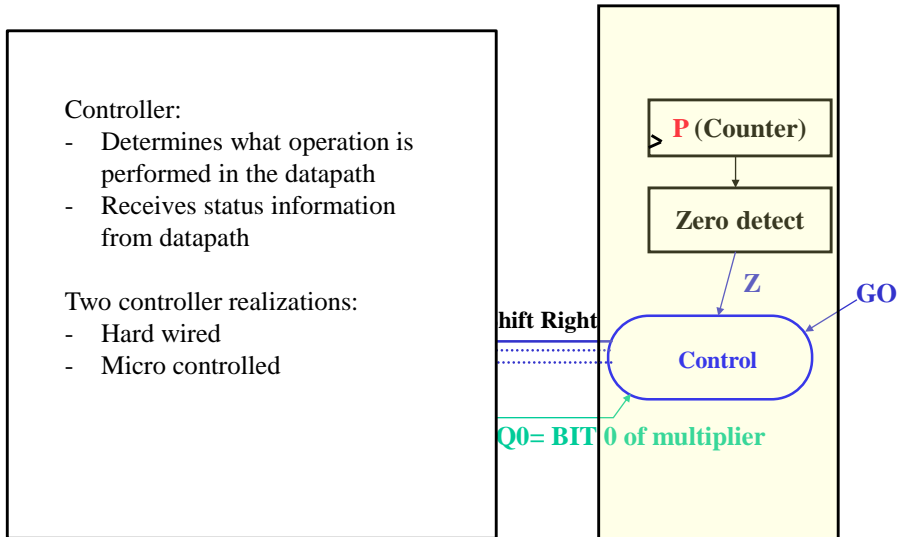


29

29

State-machine controller for multiplier

 - ▶ **State IDLE**
 - ▶ No activity in datapath
- ▶ **State INIT**
 - ▶ Initialize registers
- ▶ **State MUL0**
 - ▶ No activity in datapath. Based on Q0 next state is determined
- ▶ **State ADD**
 - ▶ Perform addition in datapath
- ▶ **State MUL1**
 - ▶ Shift product register




Note: it is assumed that addition and shifting cannot be done in the same clock cycle

30

30

Micro programmed control unit

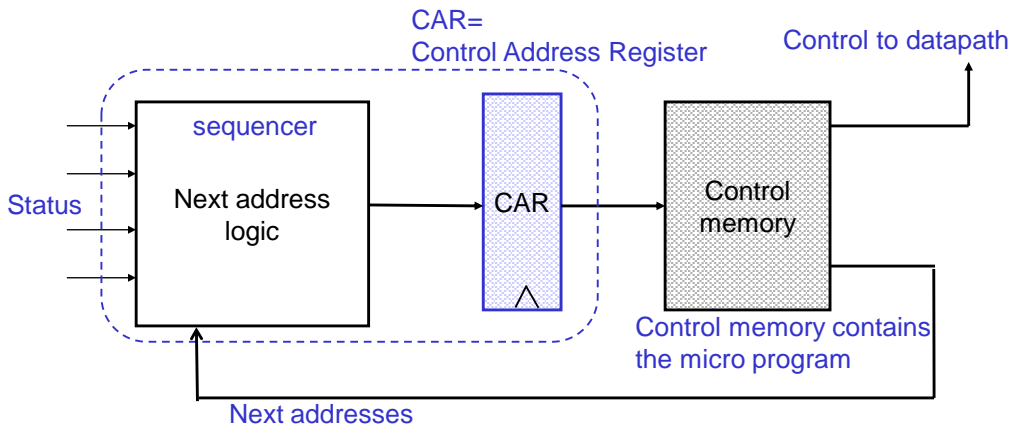


Is this a Mealy or Moore machine?

31

31


Implementation for the multiplier

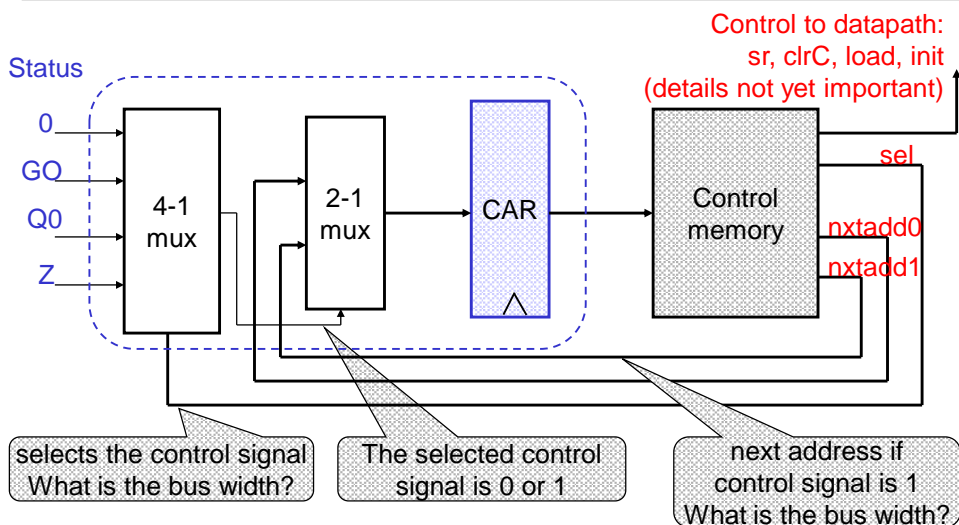

32

32

Format microinstruction

 

Sel	name	operation
00	nxt:	CAR <= nxtadd0
01	G:	IF GO=0 THEN CAR <= nxtadd0 ELSE CAR <= nxtadd1
10	Q:	IF Q0=0 THEN CAR <= nxtadd0 ELSE CAR <= nxtadd1
11	Z:	IF Z=0 THEN CAR <= nxtadd0 ELSE CAR <= nxtadd1

Datapath control	
bit 3	sr
bit 2	clrC
bit 1	load
bit 0	init


33

33

Micro program for multiplier

Microprogram in bits ('red' bits are don't care)

Address	nxtadd1	nxtadd0	SEL	datapath
000	001	000	01	0000
001	000	010	00	0101
010	011	100	10	0000
011	000	100	00	0010
100	000	010	11	1100

 

Symbolic names for readability

Address	nxtadd1	nxtadd0	SEL	datapath
idle	init	idle	Go	none
init	-	mul0	nxt	init, clrC
mul0	add	mul1	Q0	none
add	-	mul1	nxt	load
mul1	idle	mul0	Z	sr_dec_cnt, clrC

34

34

Advantages of microprogramming

- ▶ Systematic
- ▶ Changes are made in the control memory
 - ▶ Upgrade of firmware
 - Why shouldn't you interrupt the upgrade procedure of the firmware?
- ▶ Complex state machines can be implemented
- ▶ When control memory is RAM changes on-the-fly
- ▶ **Restriction** in this control unit:
 - ▶ Only 2 possible next states
 - ▶ Often 1 next address field is in the control memory and the other next address is the incremented value of CAR (e.g. ARC-processor).
 - Advantage: reduces the control memory size
 - Disadvantage: only one 'real' jump

35

35


Topics of this lecture

- ▶ **Unsigned/Signed addition**
 - ▶ Ripple carry adder
 - ▶ Status signals
- ▶ **Multiplication**
 - ▶ Unsigned
- ▶ **Components of a processor**
 - ▶ Datapath & Control
 - ▶ **Register file** ↔
 - ▶ Shifter

36

36

Simple processor

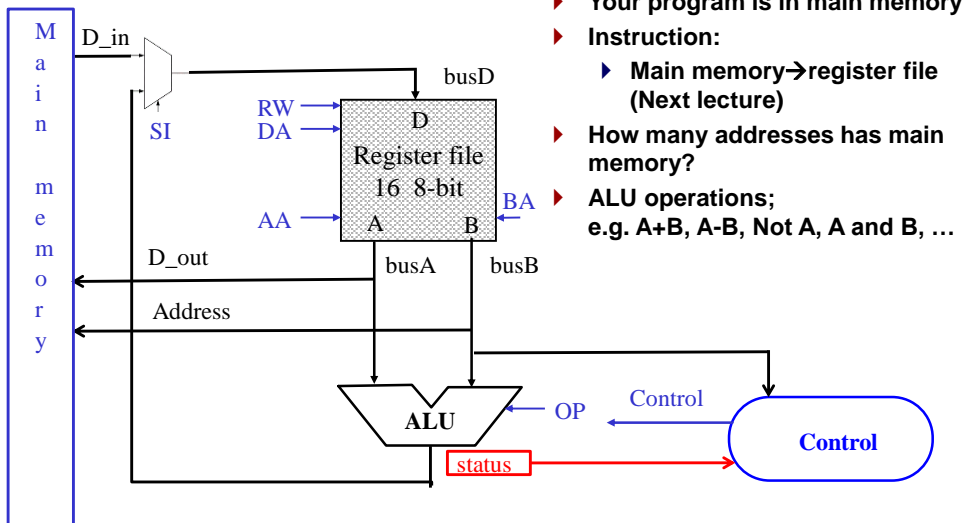


- ▶ Your program is in main memory
- ▶ Instruction:
 - ▶ Main memory → register file (Next lecture)
- ▶ How many addresses has main memory?
- ▶ ALU operations; e.g. A+B, A-B, Not A, A and B, ...

39

39

Our first program in assembly

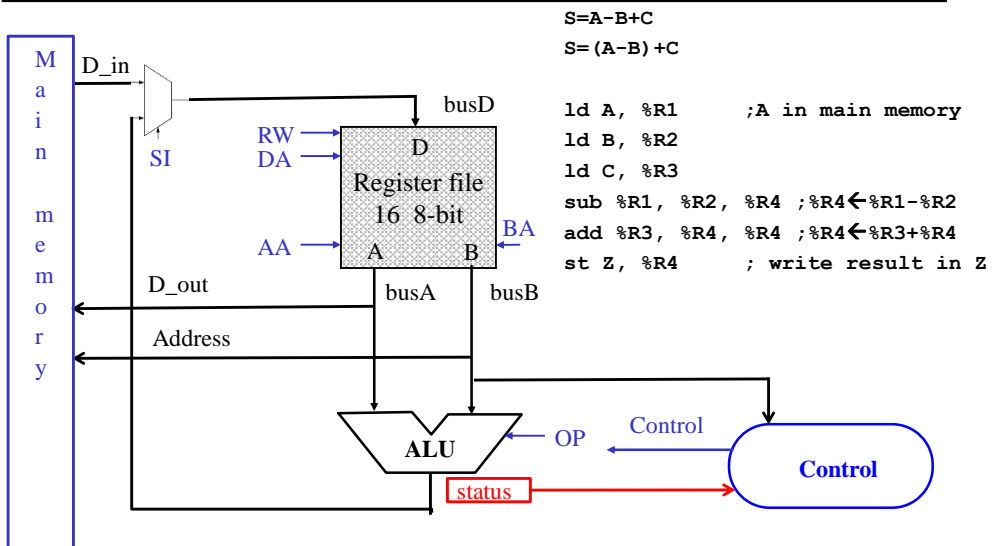

40

40

Topics of this lecture

- ▶ **Unsigned/Signed addition**
 - ▶ Ripple carry adder
 - ▶ Status signals
- ▶ **Multiplication**
 - ▶ Unsigned
- ▶ **Components of a processor**
 - ▶ Datapath & Control
 - ▶ Register file
 - ▶ **Shifter** ⇐

41

41


Example of a floating point addition

$$\boxed{-1.1100 \times 2^{-3} + 1.0000 \times 2^{-1}}$$

- ▶ Step 1: alignment of fraction (exponent the same)
 $-1.1100 \times 2^{-3} = -0.0111 \times 2^{-1}$ (shift operand)
- ▶ Step 2: add fractions
 $-0.0111 + 1.0000 = 0.1001$
- ▶ Step 3: post normalization of result
 $0.1001 \times 2^{-1} = 1.0010 \times 2^{-2}$

42

Barrel Shifter from MUXes

 

- ▶ Combinational or sequential logic?
- ▶ What comes in the MSBs?
- ▶ How many levels for 32-bit shifter?

44

44

Topics of this lecture

- ▶ Unsigned/Signed addition
 - ▶ Ripple carry adder
 - ▶ Status signals
- ▶ Multiplication
 - ▶ Unsigned
- ▶ Components of a processor
 - ▶ Datapath & Control
 - ▶ Register file
 - ▶ Shifter

45

45

Next lecture

- ▶ **Instruction Set Architecture (chapter 4)**
- ▶ **Download the ARCTools (see Canvas)**